
 




VLSI DESIGN AND AUTOMATION SUMMER INTERNSHIP



WEEK 4 SUBMISSION

RESOURCE : [WEEK 4](#) (ENC,NETLIST and DATA files are here)


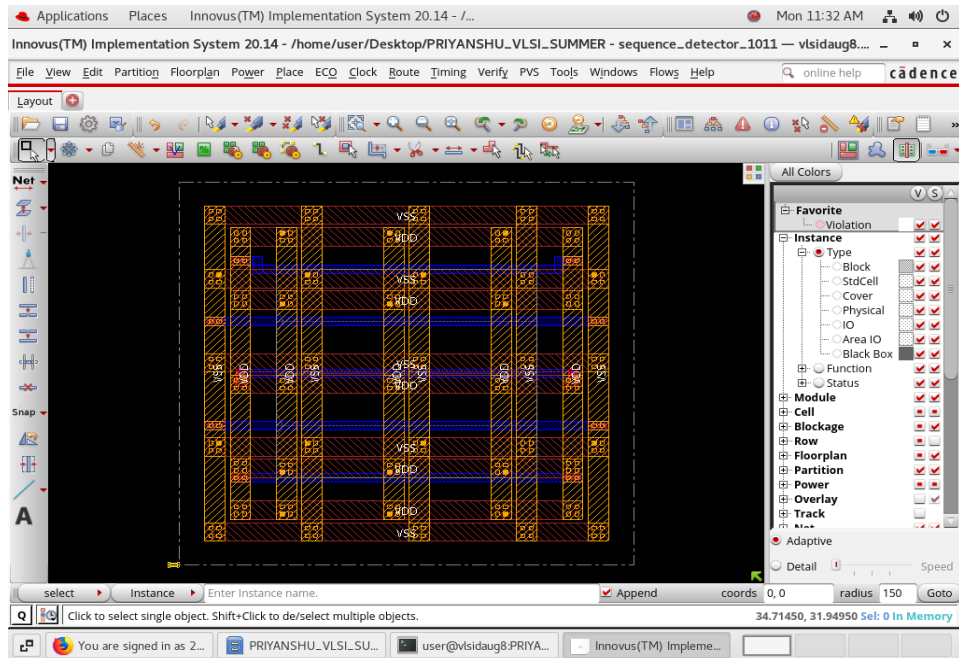
FSM (Finite State Machine) – Sequence Detector 1011





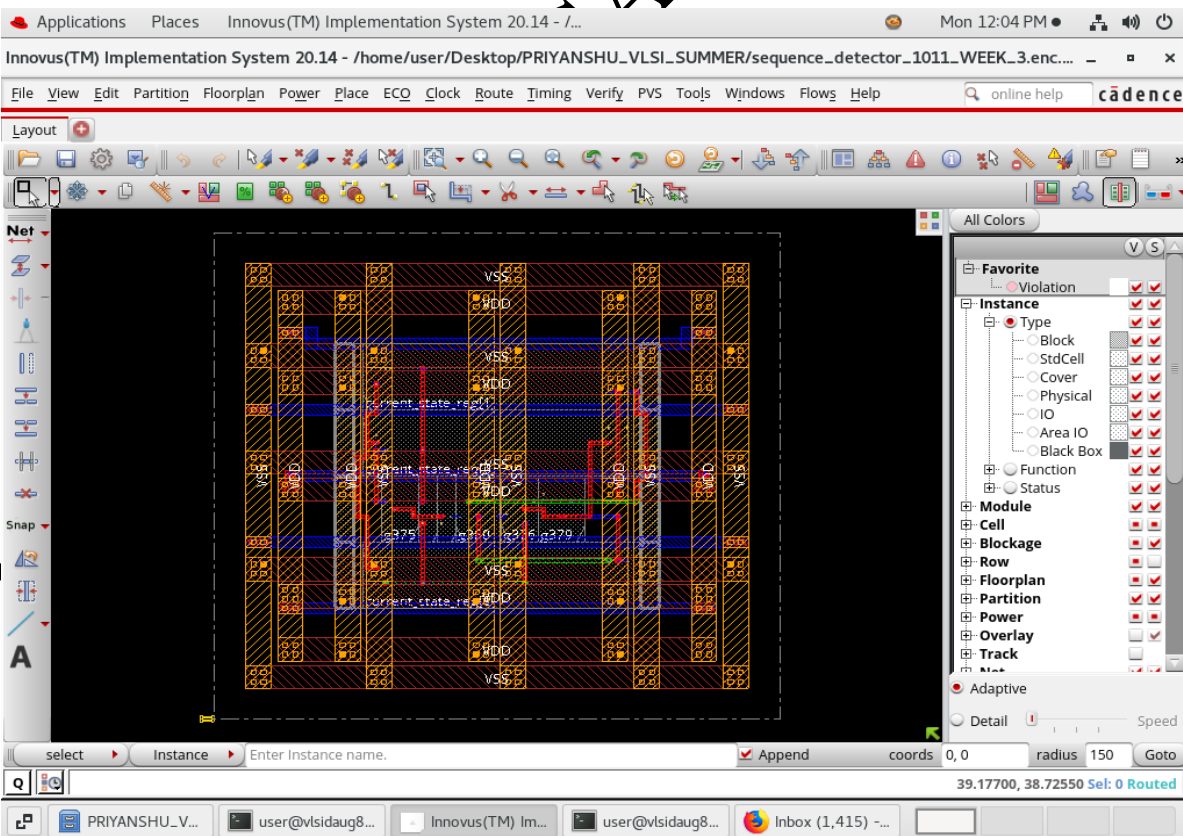
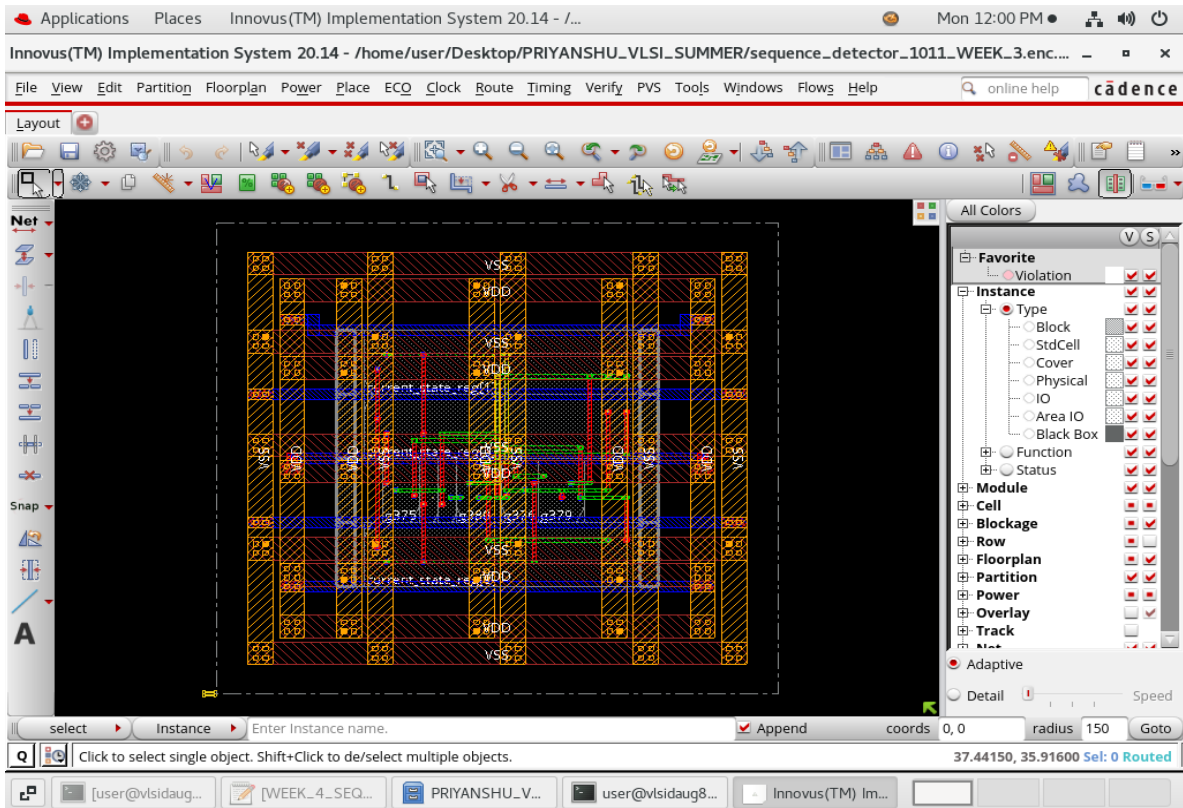


  



Combination Circuit – Full Adder

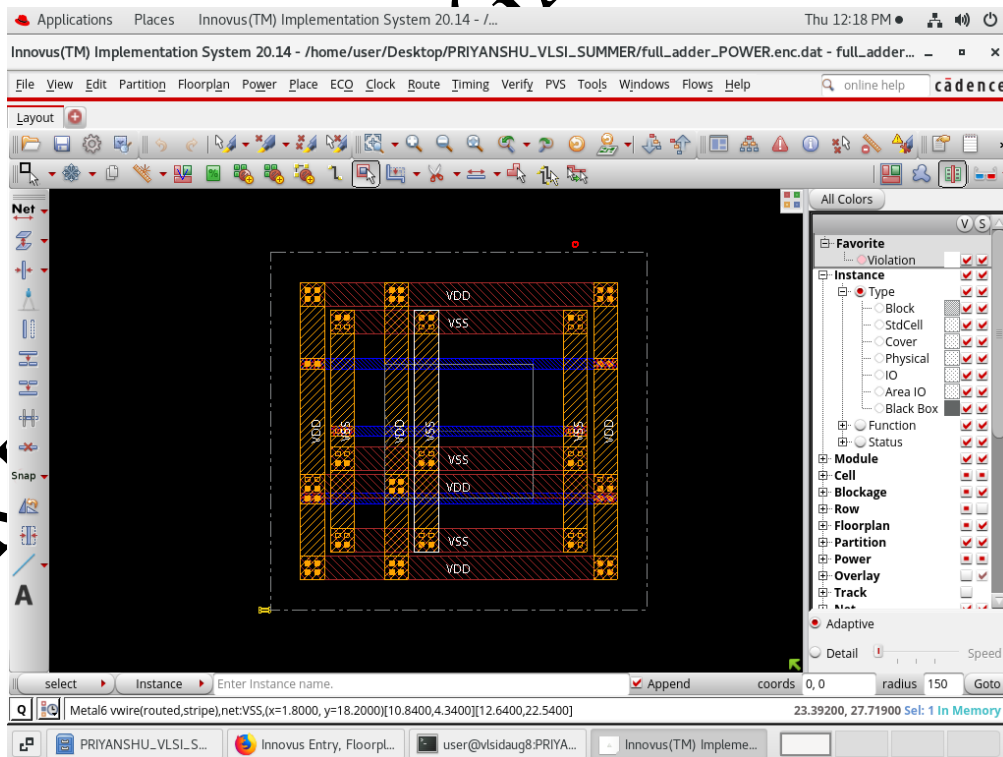
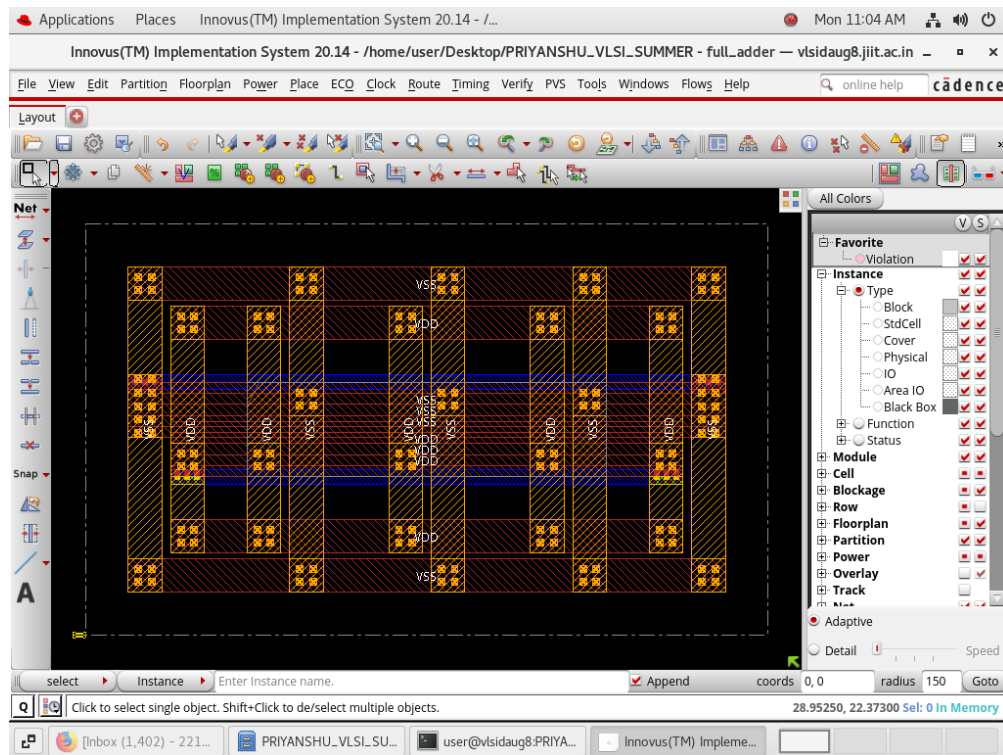


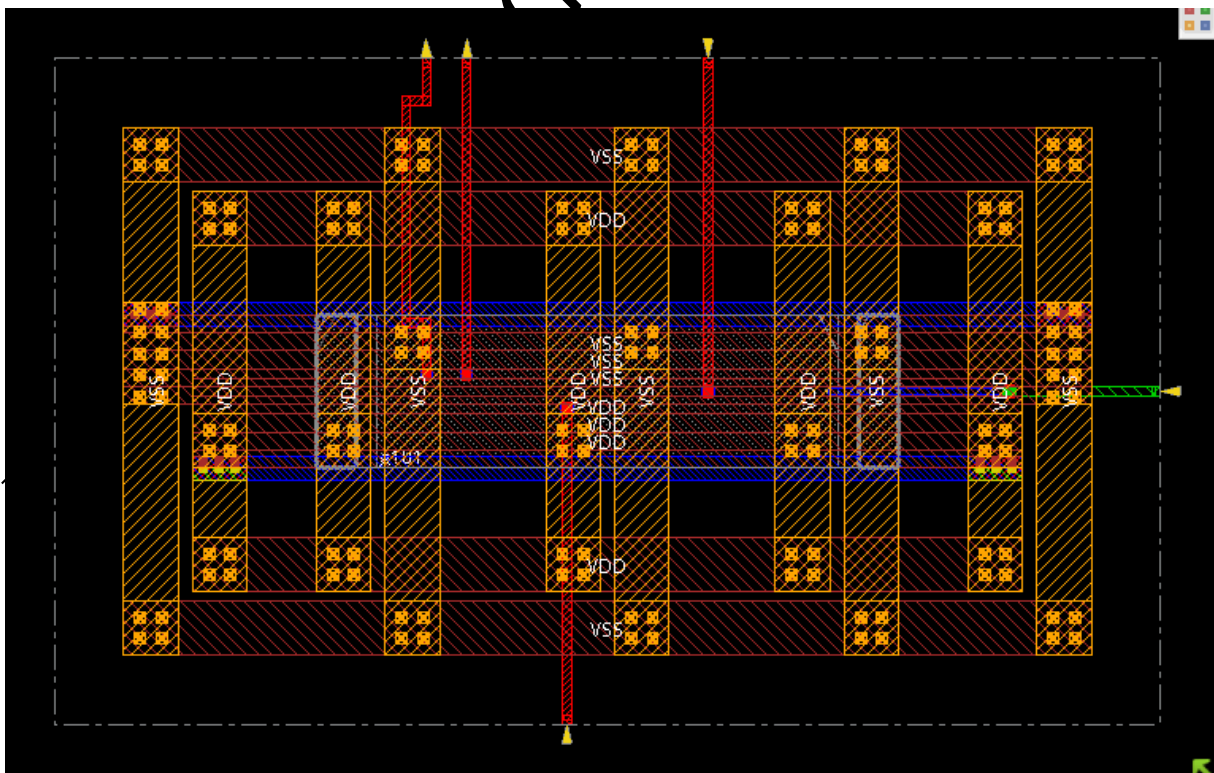
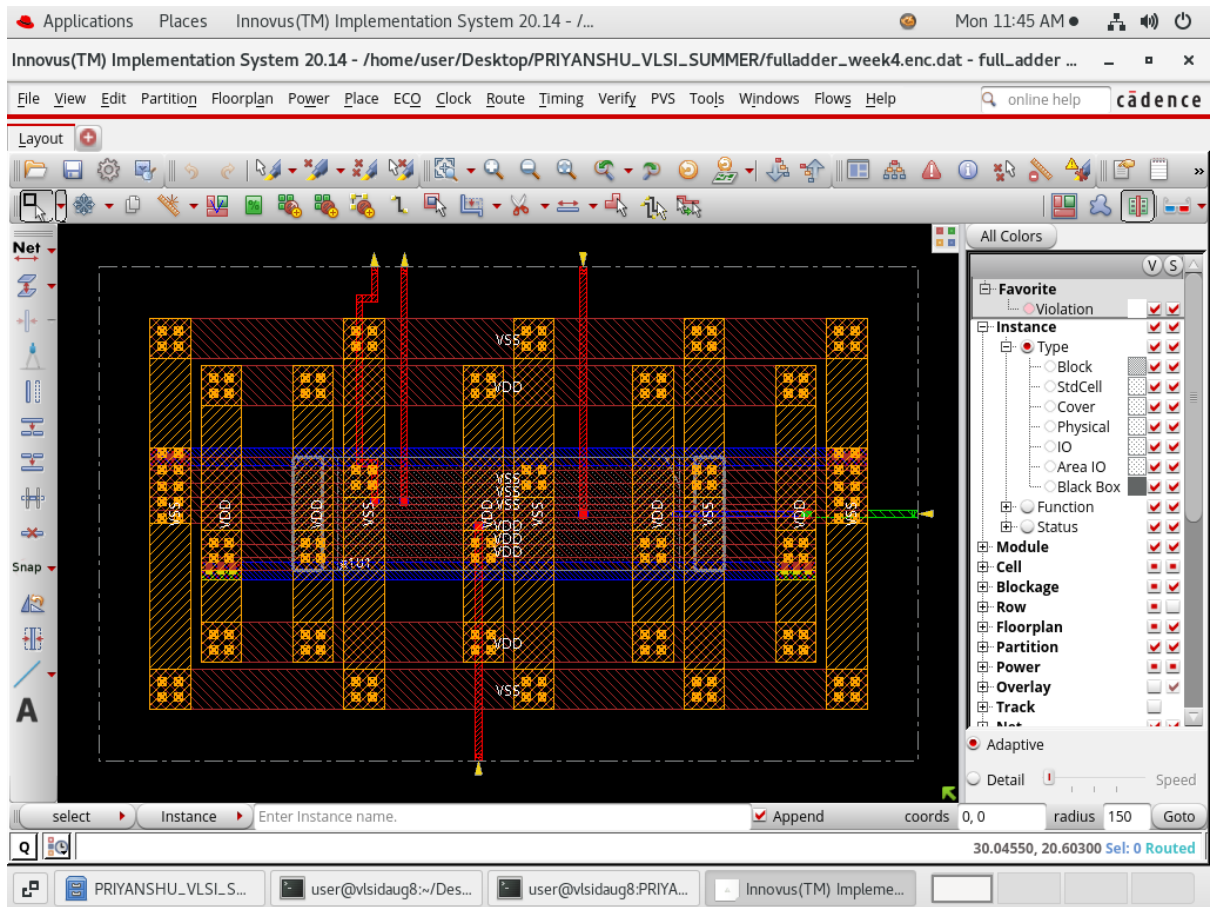


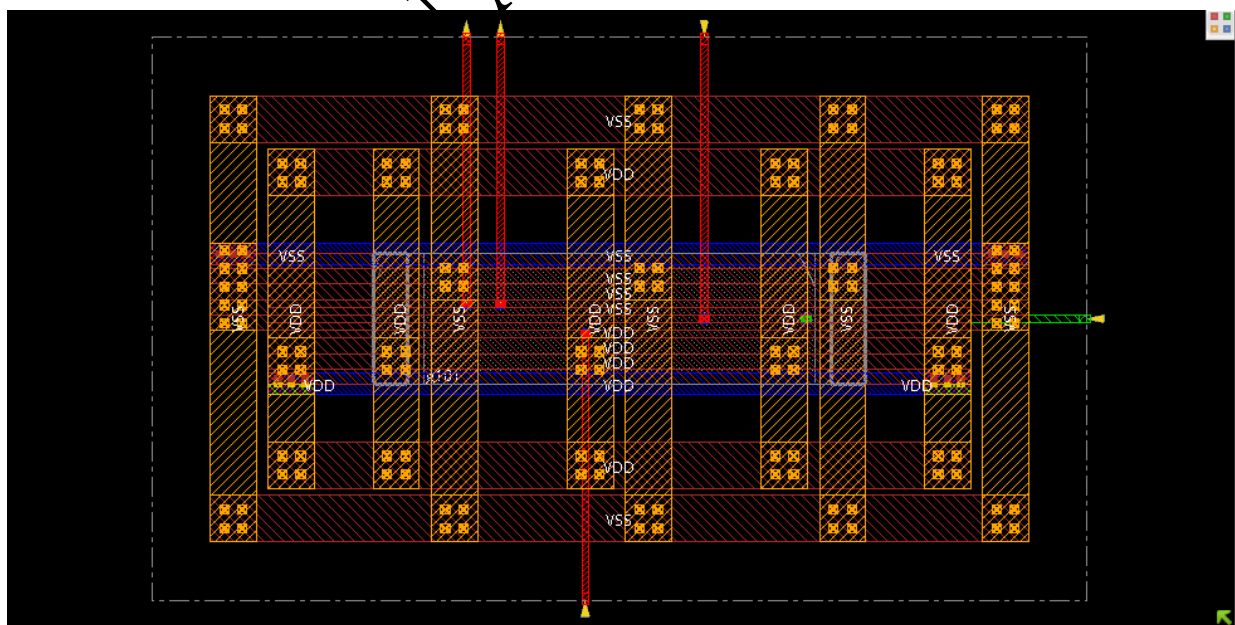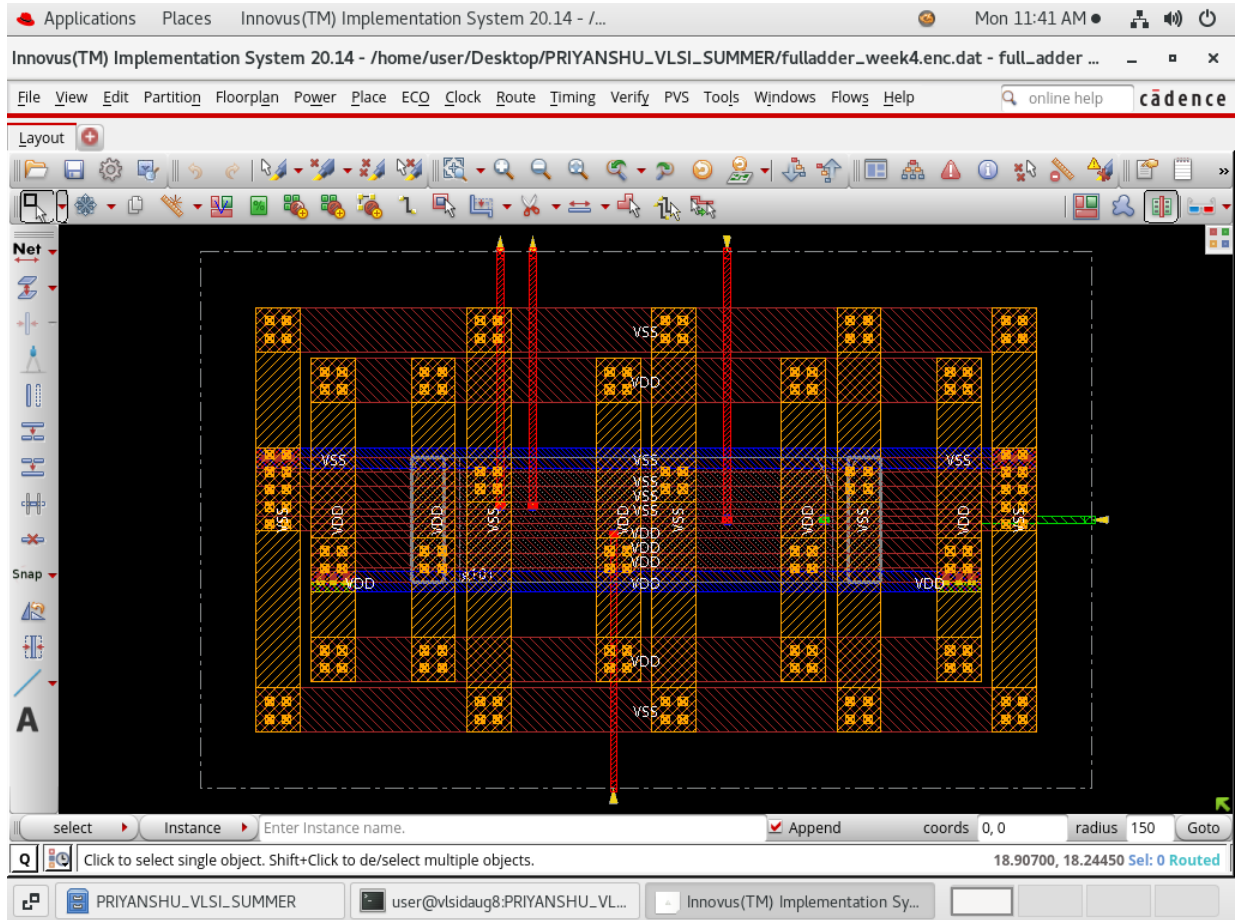

 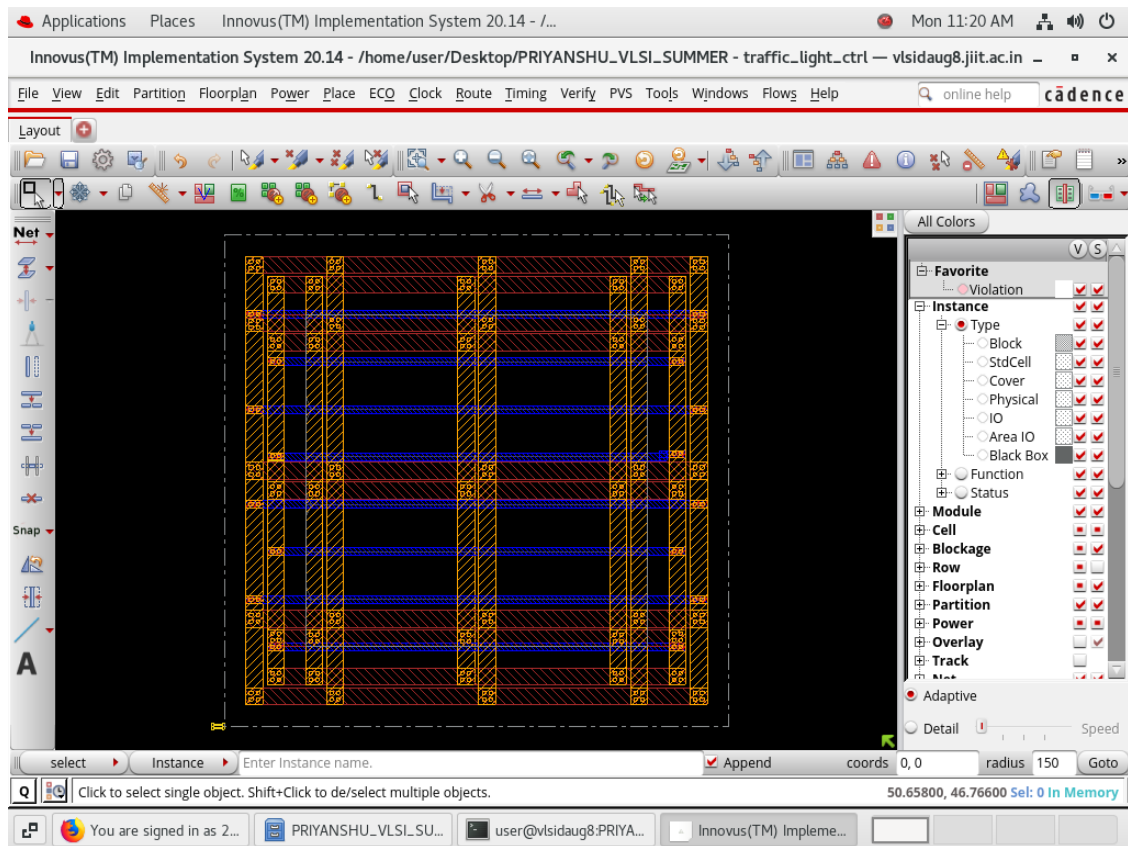Sequential Circuit – Traffic Light Control



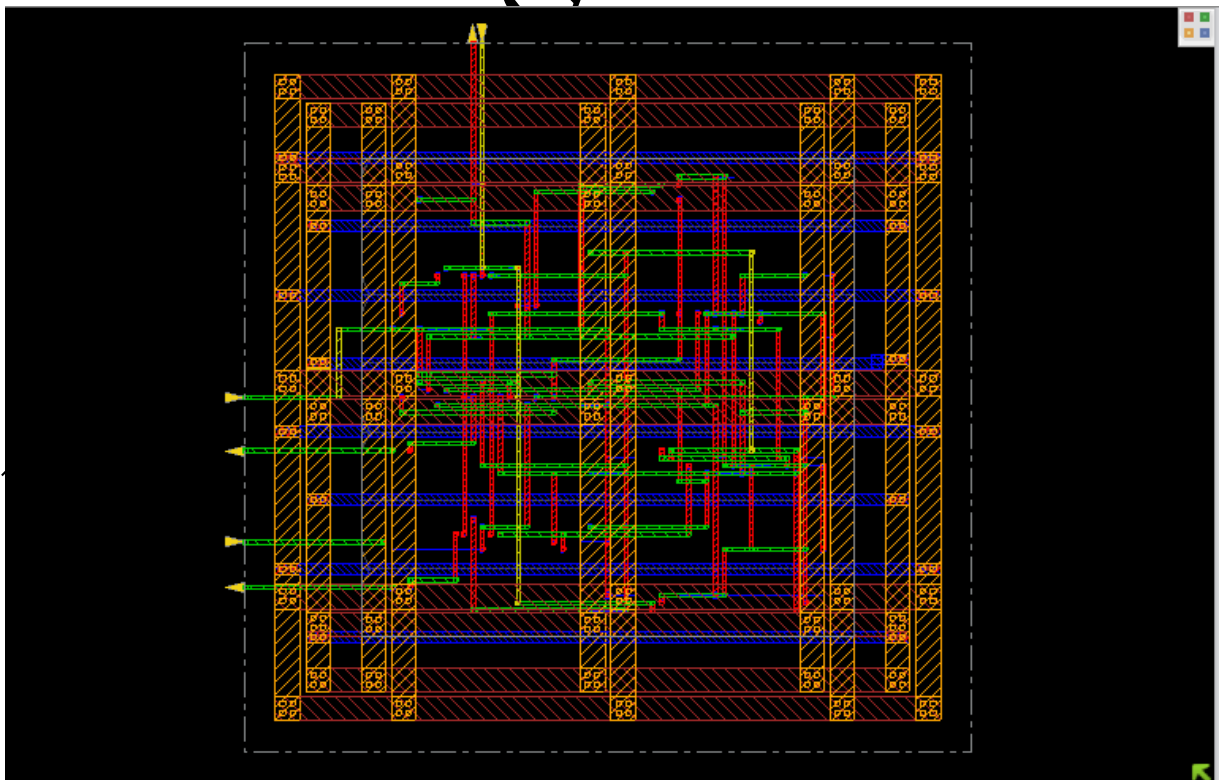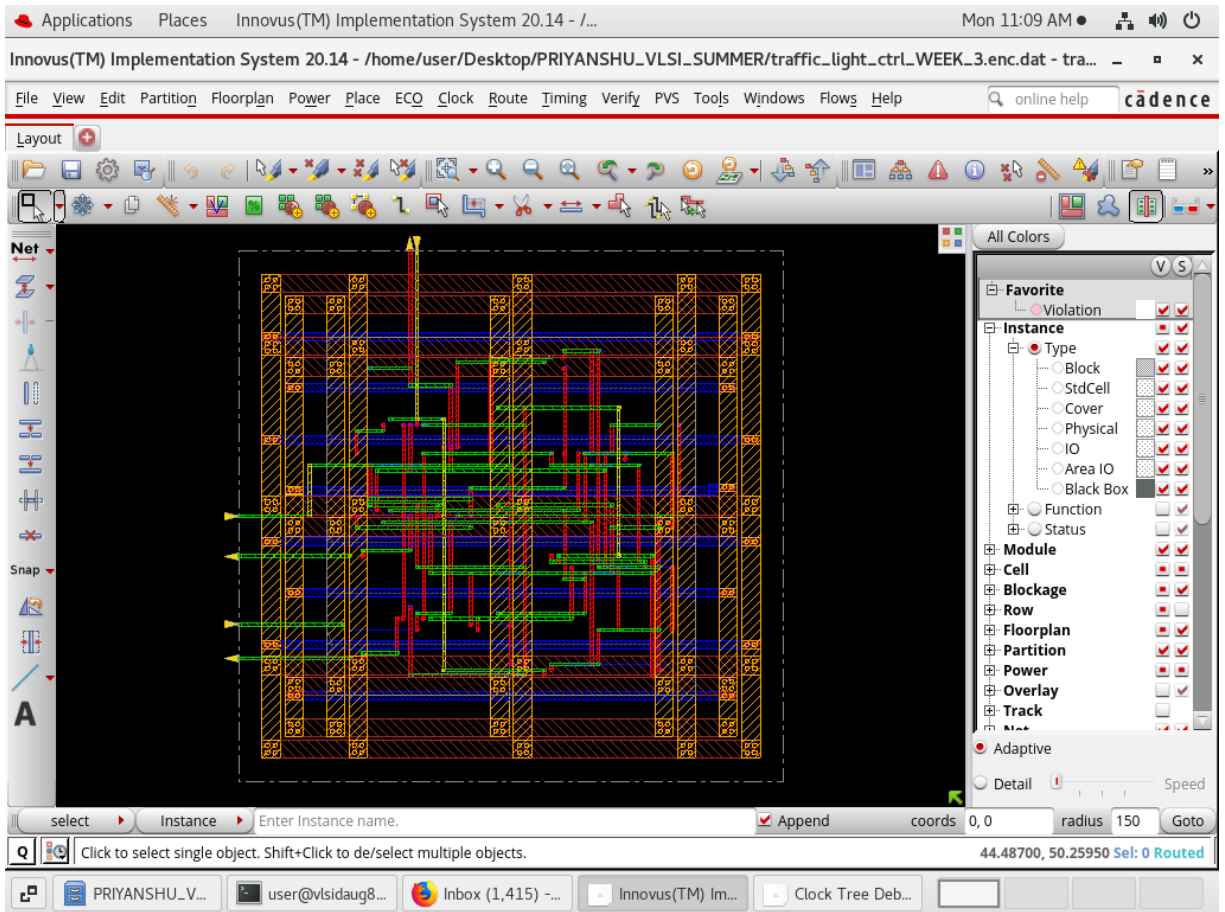

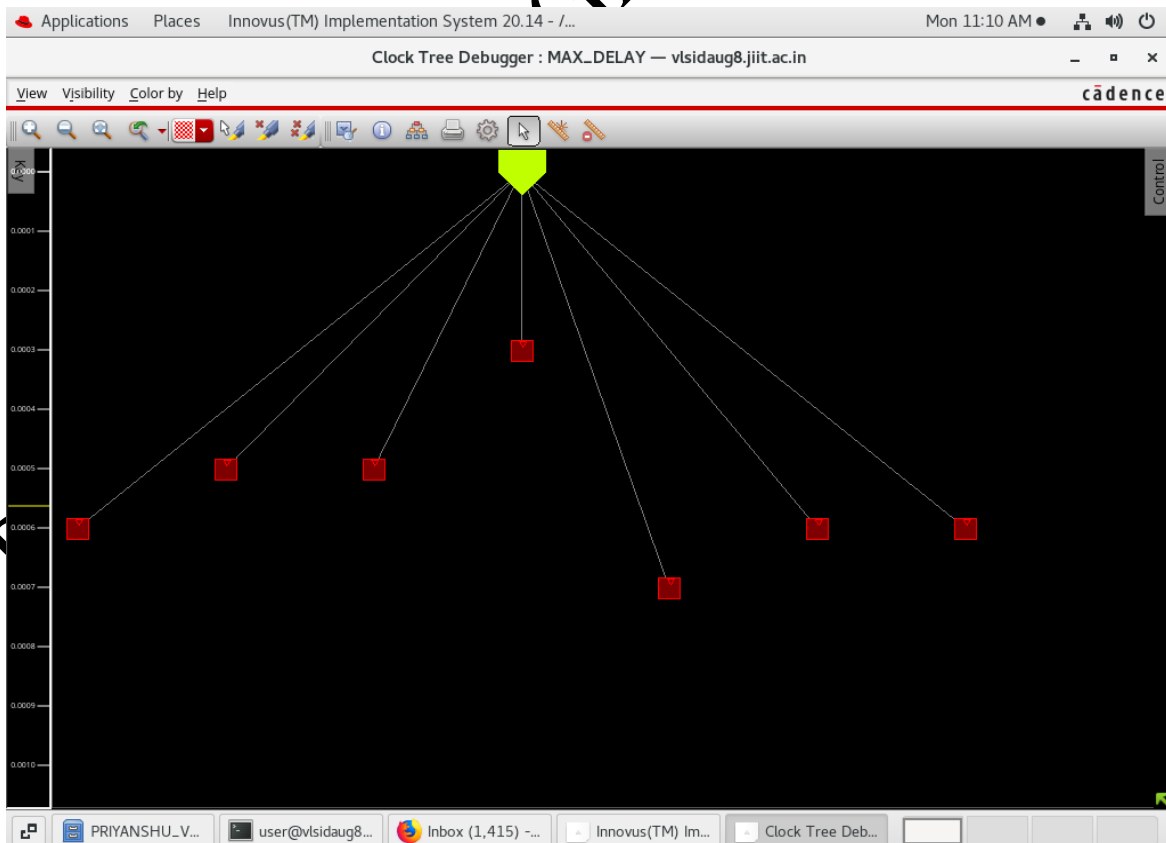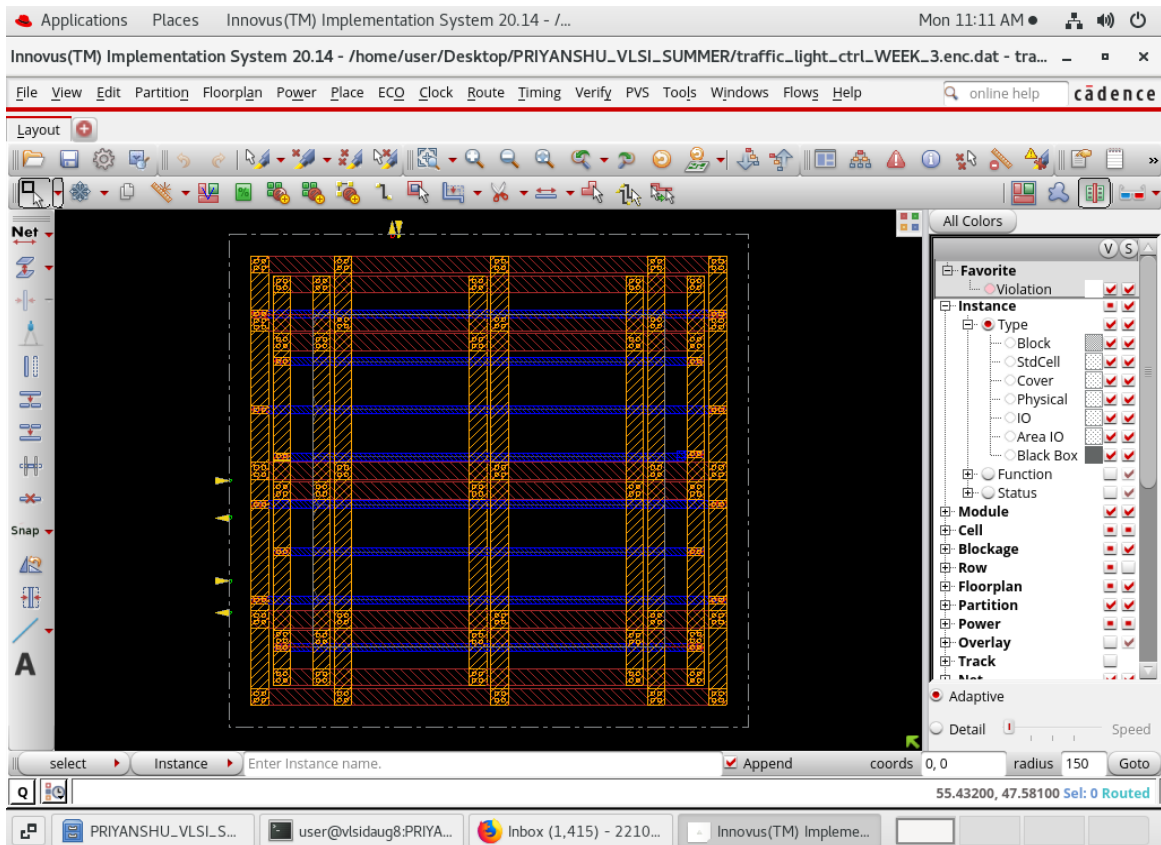

PRIYANSHU AGGARWAL 22102236