

VLSI DESIGN AND AUTOMATION SUMMER INTERNSHIP

WEEK 4 SUBMISSION

RESOURCE: [WEEK 1](#)(ENC,NETLIST and DATA files are here)

VERILOG CODE AND WAVE FORM

1. AND Gate

```
module and_gate(
```

```
input a, b,
```

```
output reg out);
```

```
always @(*) begin
```

```
if (a==1'b1 && b==1'b1)
```

```
out = 1'b1;
```

```
else
```

```
out = 1'b0;
```

```
end
```

```
endmodule
```

TB

```
module gate_and_TB();
```

```
reg a,b;
```

```
wire out;
```

```
and_gate dut(a, b, out);
```

```
initial begin
```

```
a = 0;
```

```
b = 0;
```

```
#10;
```

```
a = 0;
```

```
b = 1;
```

```
#10;
```

```
a = 1;
```

```
b = 0;
```

```
#10;
```

```
a = 1;
```


```
b = 1;
```

```
#10;
```

```
//$finish;
```

```
end
```

```
endmodule
```

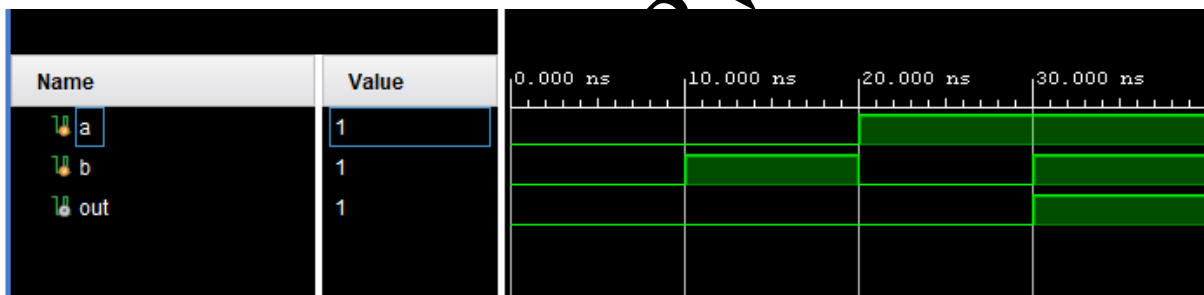

2. OR gate

```
module gate_or
```

```
input a, b;
```

```
output reg out;
```

```
always @(*) begin
```

```
if (a==1'b0 && b==1'b0)
```

```
out = 1'b0;
```

```
else
```

```
out = 1'b1;
```

```

end

endmodule

TB

module gate_or_tb;

reg a, b;


wire out;

gate_or uut (
    .a(a),
    .b(b),
    .out(out)
);

initial begin
    a = 0; b = 0; #10;
    a = 0; b = 1; #10;
    a = 1; b = 0; #10;
    a = 1; b = 1; #10;
    $finish;
end

endmodule

```

 

3. NOT gate

```

module gate_not(
    input in,
    output out);

```

```
assign out = ~in;
```

```
endmodule
```

TB

```
module gate_not_tb;
```

```
reg in;
```

```
wire out;
```

```
gate_not uut (
```

```
    .in(in),
```

```
    .out(out)
```

```
);
```

```
initial begin
```


```
    in = 0; #10;
```

```
    in = 1; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

 

4. NAND Gate

```
module nand_gate(
```

```
input a, b,
```

```
output reg out);
```

```
always @(*) begin
```

```
    if (a==1'b1 && b==1'b1)
```

```
        out = 1'b0;
```

```

else
out = 1'b1;
end
endmodule

TB

module nand_gate_tb;
reg a, b;
wire out;

nand_gate uut (
    .a(a),
    .b(b),
    .out(out)
);

initial begin
    a = 0; b = 0; #10;
    a = 0; b = 1; #10;
    a = 1; b = 0; #10;
    a = 1; b = 1; #10;
    $finish;
end
endmodule

```



5. NOR Gate

```
module gate_nor(
```

```
input a, b,
```

```
output reg out);
```

```
always @(*) begin
```

```
if (a==1'b0 && b==1'b0)
```

```
out = 1'b1;
```

```
else
```

```
out = 1'b0;
```

```
end
```

```
endmodule
```

```
TB
```

```
module gate_nor_tb;
```

```
reg a, b;
```

```
wire out;
```

```
gate_nor uut (
```

```
    .a(a),
```

```
    .b(b),
```

```
    .out(out)
```

```
);
```

```
initial begin
```

```
    a = 0; b = 0; #10;
```

```
    a = 0; b = 1; #10;
```


```
    a = 1; b = 0; #10;
```

```
    a = 1; b = 1; #10;
```

```
    $finish;
```

```
end
```

endmodule

 

6. XOR Gate

```
module gate_xor(
```

```
input a, b,
```

```
output reg out);
```

```
always @(*) begin
```

```
if ((a==1'b0 && b==1'b0) || (a==1'b1 && b==1'b1))
```

```
out = 1'b0;
```

```
else
```

```
out = 1'b1;
```

```
end
```

```
endmodule
```

```
TB
```

```
module gate_xor_tb;
```

```
reg a, b;
```

```
wire out;
```

```
gate_xor uut (
```

```
    .a(a),
```

```
    .b(b),
```

```
    .out(out)
```

```
);
```

```
initial begin
```

```
    a = 0; b = 0; #10;
```

```
    a = 0; b = 1; #10;
```


```
    a = 1; b = 0; #10;
```

```
    a = 1; b = 1; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

 

7. XNOR Gate

```
module gate_xnor(
```

```
    input a, b,
```

```
    output reg out);
```

```
    always @(*) begin
```

```
        if ((a==1'b0 && b==1'b0) || (a==1'b1 && b==1'b1))
```

```
            out = 1'b1;
```

```
        else
```

```
            out = 1'b0;
```

```
        end
```

```
    endmodule
```

```
TB
```

```
module gate_xnor_tb;
```

```
    reg a, b;
```

```
    wire out;
```



```

gate_xnor uut (
    .a(a),
    .b(b),
    .out(out)
);

```

```

initial begin
    a = 0; b = 0; #10;
    a = 0; b = 1; #10;
    a = 1; b = 0; #10;
    a = 1; b = 1; #10;
    $finish;

```

```
end
```

```
endmodule
```



8. Gate Combo

```

module gate_combo(
    input a, b,
    output out);

```

```

    wire w0, w1, w2;

```

```

    assign w0 = a^b;

```

```

    assign w1 = w0&a;

```

```

    assign w2 = w1|w0;

```

```
assign out = ~w2;
```

```
endmodule
```

```
TB
```

```
module gate_combo_tb;
```

```
reg a, b;
```

```
wire out;
```

```
gate_combo uut (
```

```
    .a(a),
```

```
    .b(b),
```

```
    .out(out)
```

```
);
```

```
initial begin
```

```
    a = 0; b = 0; #10;
```

```
    a = 0; b = 1; #10;
```


```
    a = 1; b = 0; #10;
```

```
    a = 1; b = 1; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

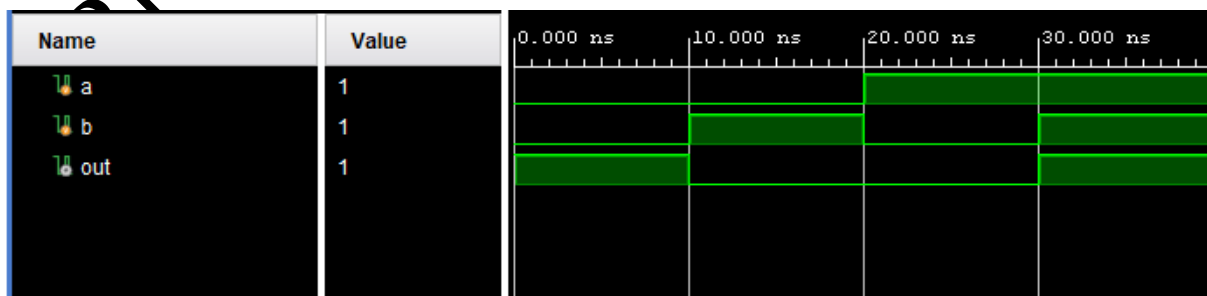

9. 4 input AND Gate

```
module and4_gate(
```

```
input a, b, c, d,  
output reg out);  
always @(*) begin  
if (a==1'b1 && b==1'b1 && c==1'b1 && d==1'b1)  
out = 1'b1;  
else  
out = 1'b0;  
end  
endmodule
```

TB

```
module and4_gate_tb;  
reg a, b, c, d;  
wire out;
```

```
and4_gate uut (  
    .a(a),  
    .b(b),  
    .c(c),  
    .d(d),  
    .out(out)  
);
```

initial begin

```
    a = 0; b = 0; c = 0; d = 0; #10;  
    a = 0; b = 1; c = 1; d = 1; #10;  
    a = 1; b = 0; c = 1; d = 1; #10;  
    a = 1; b = 1; c = 0; d = 1; #10;  
    a = 1; b = 1; c = 1; d = 0; #10;  
    a = 1; b = 1; c = 1; d = 1; #10;
```


```

    $finish;

end

endmodule

```

 

10. 4 Input OR Gate

```

module gate_4or(
input a, b, c, d,
output reg out);

```

```

always @(*) begin

```

```

if (a==1'b0 && b==1'b0 && c==1'b0 && d==1'b0)

```

```

out = 1'b0;

```

```

else

```

```

out = 1'b1;

```

```

end

```

```

endmodule

```

TB

```

module gate_4or_tb

```

```

reg a, b, c, d;

```

```

wire out;

```

```

gate_4or uut (

```

```

.a(a),

```

```

.b(b),

```

```

.c(c),

```

```

.d(d),

```

```

.out(out)

```

);

initial begin

a = 0; b = 0; c = 0; d = 0; #10;

a = 1; b = 0; c = 0; d = 0; #10;

a = 0; b = 1; c = 0; d = 0; #10;

a = 0; b = 0; c = 1; d = 0; #10;

a = 0; b = 0; c = 0; d = 1; #10;

a = 1; b = 1; c = 1; d = 1; #10;

\$finish;

end

endmodule

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns	50.000 ns
a	1						
b	1						
c	1						
d	1						
out	1						

11. Half Adder

module ha(

input a, b,

output sum, carry);

assign sum = a^b;

assign carry = a&b;

endmodule

TB

module ha_tb;

reg a, b;

wire sum, carry;

```


ha uut (
    .a(a),
    .b(b),
    .sum(sum),
    .carry(carry)
);

```

```

initial begin
    a = 0; b = 0; #10;
    a = 0; b = 1; #10;
    a = 1; b = 0; #10;
    a = 1; b = 1; #10;
    $finish;
end
endmodule

```

 

12. Full Adder

```

module fa(
    input a, b, c,
    output sum, carry);

    assign sum = a^b^c;
    assign carry = (a&b) | (b&c) | (c&a);

endmodule

```

TB

```
module fa_tb;  
reg a, b, c;  
wire sum, carry;
```

```
fa uut (
```

```
    .a(a),
```

```
    .b(b),
```

```
    .c(c),
```

```
    .sum(sum),
```

```
    .carry(carry)
```

```
);
```

```
initial begin
```

```
    a = 0; b = 0; c = 0; #10;
```

```
    a = 0; b = 0; c = 1; #10;
```

```
    a = 0; b = 1; c = 0; #10;
```

```
    a = 0; b = 1; c = 1; #10;
```

```
    a = 1; b = 0; c = 0; #10;
```

```
    a = 1; b = 0; c = 1; #10;
```


```
    a = 1; b = 1; c = 0; #10;
```

```
    a = 1; b = 1; c = 1; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

 

13. 4 Bit Ripple Carry Adder

```
module rca4(
```

```
input [3:0] a, b,  
input cin,  
output [3:0] sum,  
output cout);
```

```
wire [2:0] w;
```

```
fa u0(a[0], b[0], cin, sum[0], w[0]);  
fa u1(a[1], b[1], w[0], sum[1], w[1]);  
fa u2(a[2], b[2], w[1], sum[2], w[2]);  
fa u3(a[3], b[3], w[2], sum[3], cout);
```

```
endmodule
```

```
TB
```

```
module rca4_tb;
```

```
reg [3:0] a, b;
```

```
reg cin;
```

```
wire [3:0] sum;
```

```
wire cout;
```

```
rca4 uut (
```

```
    .a(a),
```

```
    .b(b),
```

```
    .cin(cin),
```

```
    .sum(sum),
```

```
    .cout(cout)
```

```
);
```

```
initial begin
```



```


a = 4'b0000; b = 4'b0000; cin = 0; #10;
a = 4'b0001; b = 4'b0010; cin = 0; #10;
a = 4'b0101; b = 4'b0011; cin = 1; #10;
a = 4'b1111; b = 4'b0001; cin = 0; #10;
a = 4'b1010; b = 4'b0101; cin = 1; #10;

$finish;

end

endmodule

```

 

14. 4 Bit Subtractor

```

module sub4(
    input [3:0] a, b,
    output [3:0] diff,
    output borrow
);

wire [4:0] temp;

assign temp = {1'b0, a} - {1'b0, b};
assign diff = temp[3:0];
assign borrow = temp[4];

endmodule

TB

module sub4TB;

reg [3:0] a, b;
wire [3:0] diff;

```

```
wire borrow;
```

```
sub4 uut (
```

```
    .a(a),
```

```
    .b(b),
```

```
    .diff(diff),
```

```
    .borrow(borrow)
```

```
);
```

```
initial begin
```

```
    a = 4'b0110; b = 4'b0011; #10;
```

```
    a = 4'b1000; b = 4'b0100; #10;
```

```
    a = 4'b0011; b = 4'b1000; #10;
```

```
    a = 4'b1111; b = 4'b0001; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns
> a[3:0]	f	6	8	3	f
> b[3:0]	1	3	4	8	1
> diff[3:0]	e	3	4	b	e
🔍 borrow	0				

15. 4 Bit ADDER Subtractor

```
module add_sub4(
```

```
    input [3:0] a, b,
```

```
    input sel,          // sel = 0 for addition, sel = 1 for subtraction
```

```
    output [3:0] result,
```

```
        output carry_borrow
    );

    wire [3:0] b_xor;
    wire cin;
    assign b_xor = b ^ {4{sel}}; // XOR b with sel: if sel=1, invert b (2's comp)
    assign cin = sel;
```

```
    assign {carry_borrow, result} = a + b_xor + cin;
```

```
endmodule
```

```
TB
```

```
module add_sub4TB;
```

```
    reg [3:0] a, b;
```

```
    reg sel;
```

```
    wire [3:0] result;
```

```
    wire carry_borrow;
```

```
    add_sub4 uut (
```

```
        .a(a),
```

```
        .b(b),
```

```
        .sel(sel)
```

```
        .result(result),
```

```
        .carry_borrow(carry_borrow)
```

```
    );
```

```
    initial begin
```

```
        a = 4'b0101; b = 4'b0011; sel = 0; #10; // 5 + 3
```

```


a = 4'b1000; b = 4'b0100; sel = 0; #10; // 8 + 4
a = 4'b0110; b = 4'b0011; sel = 1; #10; // 6 - 3
a = 4'b0010; b = 4'b0101; sel = 1; #10; // 2 - 5

$finish;

end

endmodule

```

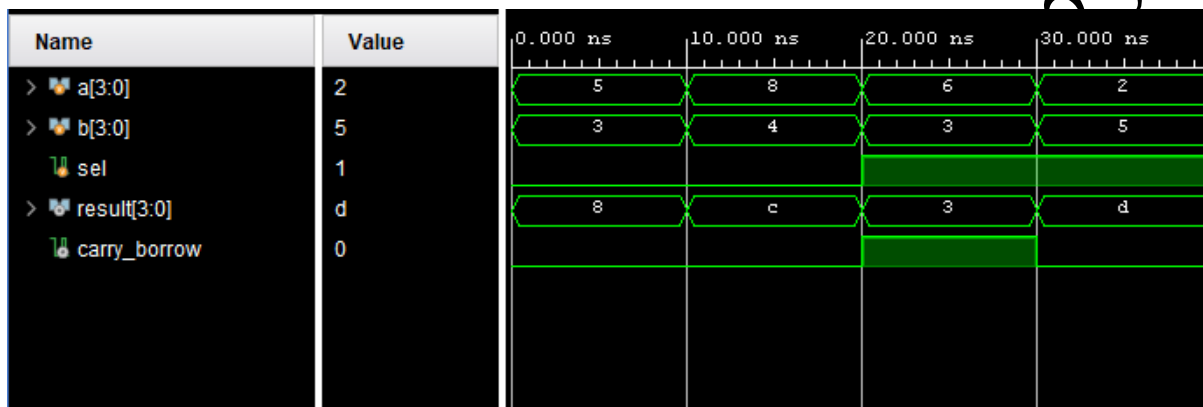

16. Mux 2X1

```

module mux_2X1(
input a, b, sel,
output q
);

assign q = (sel) ? b : a;

endmodule

TB

module mux_2X1_TB();

reg a, b, sel;

wire q;

mux_2X1 dut(a, b, sel, q);

```

initial begin

a = 0;

b = 0;

sel = 0;

#10;

a = 1;

b = 0;

sel = 0;

#10;

a = 1;

b = 0;

sel = 1;

#10;

a = 0;

b = 1;

sel = 0;

#10;

a = 0;


b = 1;

sel = 1;

#10;

end

endmodule

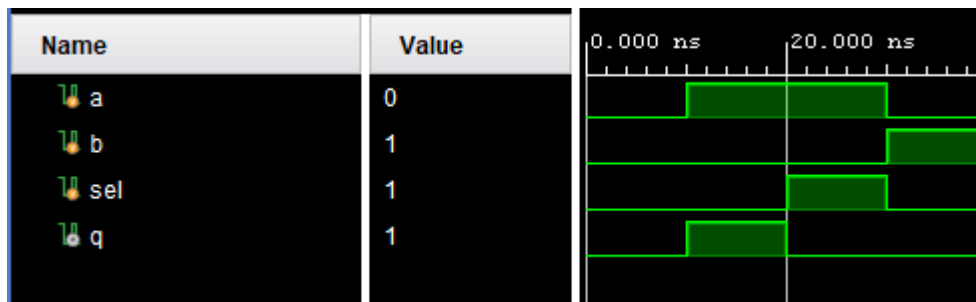

17. MUX 4X1

```
module mux_4X1(
```

```
input [3:0] in,
```

```
input [1:0] sel,
```

```
output reg q);
```

```
always @(*) begin
```

```
case (sel)
```

```
2'b00 : q = in[0];
```

```
2'b01 : q = in[1];
```

```
2'b10 : q = in[2];
```

```
2'b11 : q = in[3];
```

```
endcase
```

```
end
```

```
endmodule
```

```
TB
```

```
module mux_4X1_tb;
```

```
reg [3:0] in;
```

```
reg [1:0] sel;
```

```
wire q;
```

```
mux_4X1 uut (
```

```

.in(in),
.sel(sel),
.q(q)
);

```

```

initial begin

```

```

    in = 4'b1010;

```

```

    sel = 2'b00; #10;

```

```

    sel = 2'b01; #10;

```

```

    sel = 2'b10; #10;

```

```

    sel = 2'b11; #10;

```

```

    $finish;

```

```


end

```

```

endmodule

```

 

18. MUX 8X1

```

module mux_8X1(

```

```

    input [7:0] in,

```

```

    input [2:0] sel,

```

```

    output reg q);

```

```

always @(*) begin

```

```

    case (sel)

```

```

        3'b000 : q = in[0];

```

```
3'b001 : q = in[1];
```

```
3'b010 : q = in[2];
```

```
3'b011 : q = in[3];
```

```
3'b100 : q = in[4];
```

```
3'b101 : q = in[5];
```

```
3'b110 : q = in[6];
```


```
3'b111 : q = in[7];
```

```
endcase
```

```
end
```

```
endmodule
```

```
TB
```

 

19. DEMUX 1X2

```
module demux_1X2(
```

```
input a, sel,
```

```
output [1:0] out);
```

```
assign out = a << sel;
```

```
endmodule
```

```
TB
```

```
module demux_1X2_tb;
```

```
reg a, sel;
```

```
wire [1:0] out;
```



```


demux_1X2 uut (
    .a(a),
    .sel(sel),
    .out(out)
);

```

```

initial begin
    a = 0; sel = 0; #10;
    a = 1; sel = 0; #10;
    a = 1; sel = 1; #10;
    a = 0; sel = 1; #10;
    $finish;
end
endmodule

```

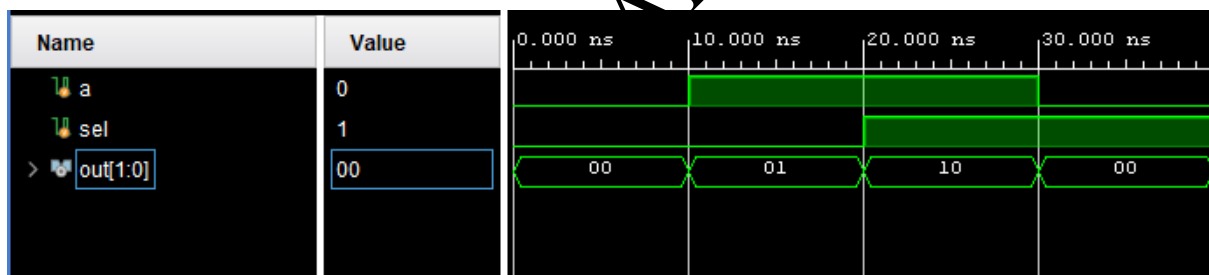

20. DEMUX 1X4

```

module demux_1X4
input a,
input [1:0] sel,
output reg [3:0] q;

//assign q = a << sel;

always @(*) begin
    case (sel)
        2'b00 : q[0] = a;

```

```
2'b01 : q[1] = a;
```

```
2'b10 : q[2] = a;
```

```
2'b11 : q[3] = a;
```

```
endcase
```

```
end
```

```
endmodule
```

```
TB
```

```
module demux_1X4_tb;
```

```
reg a;
```

```
reg [1:0] sel;
```

```
wire [3:0] q;
```

```
demux_1X4 uut (
```

```
    .a(a),
```

```
    .sel(sel),
```

```
    .q(q)
```

```
);
```

```
initial begin
```

```
    a = 1;
```

```
    sel = 2'b00; #10;
```

```
    sel = 2'b01; #10;
```

```
    sel = 2'b10; #10;
```


```
    sel = 2'b11; #10;
```

```
    a = 0; sel = 2'b10; #10;
```

```
    $finish;
```

end

endmodule

 

21. Decoder 2X4

```
module decod_2X4(
```

```
input [1:0] a,
```

```
output reg [3:0] out);
```

```
always @(*) begin
```

```
case (a)
```

```
2'b00 : out[0] = 1'b1;
```

```
2'b01 : out[1] = 1'b1;
```

```
2'b10 : out[2] = 1'b1;
```

```
2'b11 : out[3] = 1'b1;
```

```
endcase
```

```
end
```

```
endmodule
```

```
TB
```

```
module decod_2X4_tb;
```

```
reg [1:0] a;
```

```
wire [3:0] out;
```

```
decod_2X4 uut (
```

```
    .a(a),
```

```
    .out(out)
```

```
);
```

initial begin

a = 2'b00; #10;

a = 2'b01; #10;

a = 2'b10; #10;

a = 2'b11; #10;

\$finish;

end

endmodule

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns
> a[1:0]	3	0	1	2	3
> out[3:0]	f	1	3	7	f

22. Decoder 3X8

module decod_3X8(

input [2:0] a,

output [7:0] out);

assign out = 8'b00000001 << a;

endmodule

TB

module decod_3X8_tb;

reg [2:0] a;

wire [7:0] out;

decod_3X8 uut (

.a(a),

.out(out)

);

initial begin

a = 3'b000; #10;

a = 3'b001; #10;

a = 3'b010; #10;

a = 3'b011; #10;

a = 3'b100; #10;

a = 3'b101; #10;


a = 3'b110; #10;

a = 3'b111; #10;

\$finish;

end

endmodule

 

23. Encoder 4X2

module encod_4X2(

input [3:0] a,

output reg [1:0] out);

always @(*) begin

case (a)

4'b0001 : out = 2'b00;

4'b0010 : out = 2'b01;

4'b0100 : out = 2'b10;

4'b1000 : out = 2'b11;

default : out = 2'b00;

endcase

```

end

endmodule

TB

module encod_4X2_tb;

reg [3:0] a;


wire [1:0] out;

encod_4X2 uut (
    .a(a),
    .out(out)
);

initial begin
    a = 4'b0001; #10;
    a = 4'b0010; #10;
    a = 4'b0100; #10;
    a = 4'b1000; #10;
    a = 4'b0000; #10;
    a = 4'b1111; #10;
    $finish;
end

endmodule

```

 

24. Encoder 8X3

```

module encod_8X3(
    input [7:0] a,
    output reg [2:0] out);

```

```
always @(*) begin
```

```
case (a)
```

```
8'b00000001 : out = 3'b000;
```

```
8'b00000010 : out = 3'b001;
```

```
8'b00000100 : out = 3'b010;
```

```
8'b00001000 : out = 3'b011;
```

```
8'b00010000 : out = 3'b100;
```

```
8'b00100000 : out = 3'b101;
```

```
8'b01000000 : out = 3'b110;
```

```
8'b10000000 : out = 3'b111;
```

```
default : out = 3'b000;
```

```
endcase
```

```
end
```

```
endmodule
```

```
TB
```

```
module encod_8X3_tb;
```

```
reg [7:0] a;
```

```
wire [2:0] out;
```

```
encod_8X3 uut
```

```
.a(a),
```

```
.out(out)
```

```
);
```

```
initial begin
```

```
    a = 8'b00000001; #10;
```

```
    a = 8'b00000010; #10;
```

```
    a = 8'b00000100; #10;
```

```


a = 8'b00001000; #10;
a = 8'b00010000; #10;
a = 8'b00100000; #10;
a = 8'b01000000; #10;
a = 8'b10000000; #10;
a = 8'b00000000; #10;
a = 8'b11111111; #10;

$finish;

end

endmodule

```

 

25. Priority Encoder 8X3

```

module pencod_8X3(
input [7:0] a,
output reg [2:0] out);

always @(*) begin
casez (a)
8'b00000000 : out = 3'b000;
8'b00000001 : out = 3'b000;
8'b00000010 : out = 3'b001;
8'b00000011 : out = 3'b010;
8'b000001?? : out = 3'b011;
8'b00001??? : out = 3'b100;
8'b0001???? : out = 3'b101;
8'b01?????? : out = 3'b110;
8'b1??????? : out = 3'b111;

```



```
endcase
```

```
end
```

```
endmodule
```

```
TB
```

```
module pencod_8X3_tb;
```

```
reg [7:0] a;
```

```
wire [2:0] out;
```

```
pencod_8X3 uut(a, out);
```

```
initial begin
```

```
    a = 8'b00000000; #10;
```

```
    a = 8'b00000001; #10;
```

```
    a = 8'b00000010; #10;
```

```
    a = 8'b00000100; #10;
```

```
    a = 8'b00001000; #10;
```

```
    a = 8'b00010000; #10;
```

```
    a = 8'b00100000; #10;
```

```
    a = 8'b01000000; #10;
```

```
    a = 8'b10000000; #10;
```

```
    a = 8'b11111111; #10;
```

```
    a = 8'b00000011; #10;
```

```
    a = 8'b00000111; #10;
```

```
    a = 8'b00001111; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns	50.000 ns	60.000 ns	70.000 ns	80.000 ns	90.000 ns	100.000 ns	110.000 ns	120.000 ns
a[7:0]	00001111	00000000	00000001	00000010	00000100	00001000	00100000	01000000	10000000	11111111	00000011	00000111	00001111	
b[2:0]	011	000	001	010	011	100	101	110		111	001	010	011	

26. 1 Bit Comparator

```
module comp1(
```

```
input a, b,
```

```
output reg l,e, g);
```

```
initial begin
```

```
e = 0;
```

```
l = 0;
```

```
g = 0;
```

```
end
```

```
always @(*) begin
```

```
if (a > b) begin
```

```
g = 1'b1; l = 0; e = 0;
```

```
end
```

```
else if ( a < b) begin
```

```
l = 1; g = 0; e = 0;
```

```
end
```

```
else
```

```
e = 1; g = 0; l = 0;
```

```
end
```

```
endmodule
```

```
TB
```

```
module comp1_tb;
```

```
reg a, b;
```

```
wire l, e, g;
```

```
comp1 uut(a, b, l, e, g);
```

initial begin

a = 0; b = 0; #10;

a = 0; b = 1; #10;


a = 1; b = 0; #10;

a = 1; b = 1; #10;

\$finish;

end

endmodule

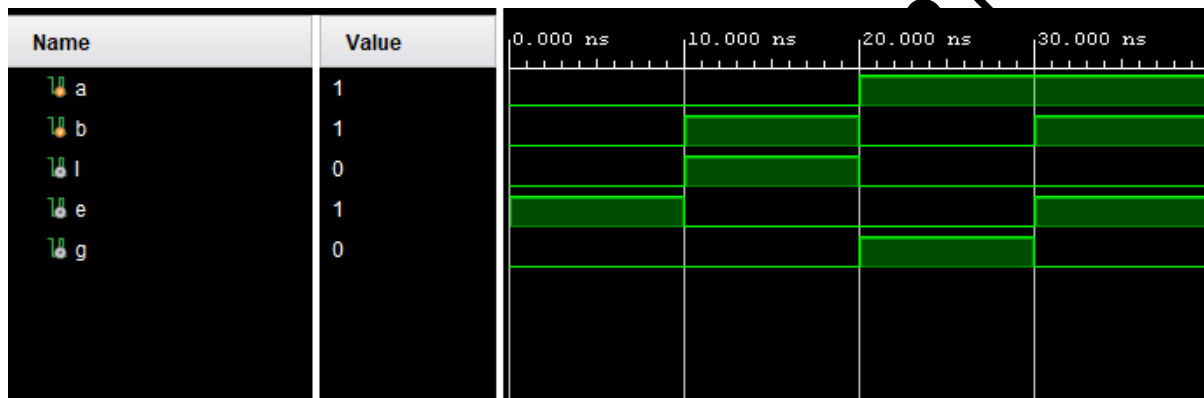

27. 2 Bit Comparator

module comp2(

input [1:0] a,b,

output reg l,e,g);

always @(*) begin

if (a>b) begin

g = 1;

l = 0;

e = 0;

end

else if (a<b) begin

l = 1;

```
g = 0;
e = 0;
end
else begin
e = 1;
l = 0;
g = 0;
end
end
```

```
endmodule
```

```
TB
```

```
module comp2_tb;
```

```
reg [1:0] a, b;
```

```
wire l, e, g;
```

```
comp2 uut(a, b, l, e, g);
```

```
initial begin
```

```
a = 2'b00; b = 2'b00; #10;
```

```
a = 2'b00; b = 2'b01; #10;
```

```
a = 2'b01; b = 2'b00; #10;
```

```
a = 2'b10; b = 2'b10; #10;
```


```
a = 2'b11; b = 2'b10; #10;
```

```
a = 2'b10; b = 2'b11; #10;
```

```
$finish;
```

```
end
```

```
endmodule
```

 

28. 4 Bit Comparator

```
module comp4(
```

```
input [3:0] a,b,
```

```
output reg l,e,g );
```

```
always @(*) begin
```

```
if (a>b) begin
```

```
g = 1;
```

```
l = 0;
```

```
e = 0;
```

```
end
```

```
else if (a<b) begin
```

```
l = 1;
```

```
g = 0;
```

```
e = 0;
```

```
end
```

```
else begin
```

```
e = 1;
```

```
l = 0;
```

```
g = 0;
```

```
end
```

```
end
```

```
endmodule
```

```
TB
```

```

module comp4_tb;

reg [3:0] a, b;

wire l, e, g;

comp4 uut(a, b, l, e, g);

```

```

initial begin

```

```

    a = 4'b0000; b = 4'b0000; #10;

```

```

    a = 4'b0010; b = 4'b0001; #10;

```

```

    a = 4'b0001; b = 4'b0010; #10;

```

```

    a = 4'b1111; b = 4'b1111; #10;

```

```

    a = 4'b1001; b = 4'b0110; #10;

```

```

    a = 4'b0011; b = 4'b1010; #10;

```

```

    $finish;

```

```


end

```

```

endmodule

```

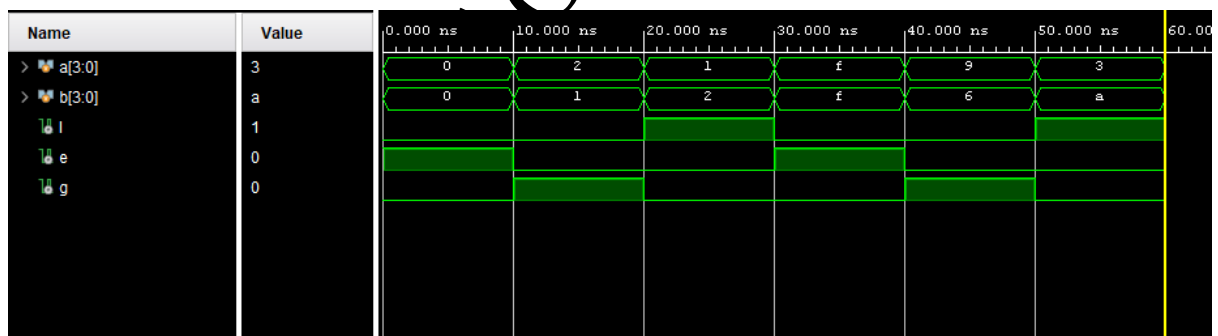

29. 8 Bit Comparator

```

module comp8(
input [7:0] a,b,
output reg l,e,g );

```

```

always @(*) begin

```

```

    if (a>b) begin

```

```
g = 1;
l = 0;
e = 0;
end
else if (a<b) begin
l = 1;
g = 0;
e = 0;
end
else begin
e = 1;
l = 0;
g = 0;
end
end

endmodule

TB
module comp8_tb;
reg [7:0] a, b;
wire l, e, g;

comp8 uut(a, b, l, e, g);

initial begin
    a = 8'd0;  b = 8'd0;  #10;
    a = 8'd45; b = 8'd32; #10;
    a = 8'd10; b = 8'd75; #10;
    a = 8'd255; b = 8'd255; #10;
```

```

a = 8'd100; b = 8'd99; #10;


a = 8'd5; b = 8'd120; #10;

$finish;

end

endmodule

```

 

30. Greater Than Comparator

```

module compgt(
input [7:0] a,b,
output reg g );

always @(*) begin
if (a>b)
g = 1;

else
g = 0;
end

endmodule

```

```

TB

module compgt_tb;

reg [7:0] a, b;

wire l, e, g;

```



```
compgt uut(a, b, l, e, g);
```

```
initial begin
```

```
    a = 8'd0; b = 8'd0; #10;
```

```
    a = 8'd45; b = 8'd32; #10;
```

```
    a = 8'd10; b = 8'd75; #10;
```

```
    a = 8'd255; b = 8'd255; #10;
```

```
    a = 8'd100; b = 8'd99; #10;
```

```
    a = 8'd5; b = 8'd120; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns	50.000 ns
> a[7:0]	05	00	2d	0a	ff	64	05
> b[7:0]	78	00	20	4b	ff	63	78
g	0						

31. 4 Bit Carry Look Ahead Adder

```
module cla4 (
```

```
    input [3:0] a, b,
```

```
    input cin,
```

```
    output [3:0] sum,
```

```
    output cout
```

```
);
```

```
    wire [3:0] g, p, c;
```

```
    assign g = a & b;
```

```
    assign p = a ^ b;
```

```

assign c[0] = cin;

assign c[1] = g[0] | (p[0] & c[0]);

assign c[2] = g[1] | (p[1] & g[0]) | (p[1] & p[0] & c[0]);

assign c[3] = g[2] | (p[2] & g[1]) | (p[2] & p[1] & g[0]) | (p[2] & p[1] & p[0] & c[0]);


assign sum = p ^ c;

assign cout = g[3] | (p[3] & g[2]) | (p[3] & p[2] & g[1]) |
              (p[3] & p[2] & p[1] & g[0]) |
              (p[3] & p[2] & p[1] & p[0] & cin);

```

Endmodule

TB

```
module cla4_TB;
```

```
    reg [3:0] a, b;
```

```
    reg cin;
```

```
    wire [3:0] sum;
```

```
    wire cout;
```

```
    cla4 uut (
```

```
        .a(a), .b(b), .cin(cin),
```

```
        .sum(sum), .cout(cout)
```

```
    );
```

```
    initial begin
```

```
        a = 4'b0000; b = 4'b0000; cin = 0;
```

```
        #10 a = 4'b0001; b = 4'b0001; cin = 0;
```

```
        #10 a = 4'b0011; b = 4'b0101; cin = 1;
```

```
        #10 a = 4'b1111; b = 4'b0001; cin = 0;
```

```
        #10 a = 4'b1010; b = 4'b0101; cin = 1;
```

```
        #10 $finish;
```

end

endmodule

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns
> a[3:0]	a	0	1	3	f	a
> b[3:0]	5	0	1	5	1	5
cin	1					
> sum[3:0]	0	0	2	9	0	
cout	1					

32. 4 Bit Binary Multiplier

module mult4 (

input [3:0] a, b,

output [7:0] product

);

wire [7:0] p0 = b[0] ? {4'b0000, a} : 8'b0;

wire [7:0] p1 = b[1] ? {3'b000, a, 1'b0} : 8'b0;

wire [7:0] p2 = b[2] ? {2'b00, a, 2'b00} : 8'b0;

wire [7:0] p3 = b[3] ? {1'b0, a, 3'b000} : 8'b0;

assign product = p0 + p1 + p2 + p3;

endmodule

TB

module mult4_TB;

reg [3:0] a, b;

wire [7:0] product;

mult4 uut (

.a(a), .b(b),

.product(product)

);

initial begin

a = 4'b0000; b = 4'b0000;

#10 a = 4'b0010; b = 4'b0011;

#10 a = 4'b1111; b = 4'b0001;

#10 a = 4'b1010; b = 4'b0101;

#10 a = 4'b1111; b = 4'b1111;

#10 \$finish;

end

endmodule

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns
> a[3:0]	f	0	2	f	a	f
> b[3:0]	f	0	3	1	5	f
> product[7:0]	e1	00	06	0f	32	e1

33. Booth Multiplier

module booth_multiplier (

input [3:0] multiplicand,

input [3:0] multiplier,

output [7:0] product

);

reg [7:0] A, S, P;

reg [3:0] M, Q;

integer i;

always @(*) begin

A = {multiplicand, 4'b0000};

S = {~multiplicand + 1'b1, 4'b0000};

```

P = {4'b0000, multiplier, 1'b0};

for (i = 0; i < 4; i = i + 1) begin
    case (P[1:0])
        2'b01: P = P + A;
        2'b10: P = P + S;
        default: P = P;
    endcase
    P = {P[7], P[7:1]}; // arithmetic right shift
end
end

assign product = P[7:0];
endmodule

TB
module booth_multiplier_TB;
    reg [3:0] multiplicand, multiplier;
    wire [7:0] product;

    booth_multiplier uut (
        .multiplicand(multiplicand),
        .multiplier(multiplier),
        .product(product)
    );

    initial begin
        multiplicand = 4'd3; multiplier = 4'd2; #10;
        multiplicand = 4'd4; multiplier = 4'd3; #10;
        multiplicand = 4'd7; multiplier = 4'd5; #10;
    end
endmodule

```

```

multiplicand = 4'd8; multiplier = 4'd8; #10;

multiplicand = 4'd15; multiplier = 4'd15; #10;

$finish;

end

endmodule

```

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns
> multiplicand[3:0]	f	3	4	7	8	f
> multiplier[3:0]	f	2	3	5	8	f
> product[7:0]	fa	06	0c	eb	c1	fa

34. Array Multiplier

```

module array_multiplier (
    input [3:0] a,
    input [3:0] b,
    output [7:0] product
);

    wire [3:0] p0, p1, p2, p3;
    wire [7:0] s1, s2, s3;

    assign p0 = a & {4{b[0]}};
    assign p1 = a & {4{b[1]}};
    assign p2 = a & {4{b[2]}};
    assign p3 = a & {4{b[3]}};

    assign s1 = {1'b0, p1, 1'b0}; // shifted left by 1
    assign s2 = {2'b0, p2, 2'b0}; // shifted left by 2
    assign s3 = {3'b0, p3, 3'b0}; // shifted left by 3

    assign product = {4'b0000, p0} + s1 + s2 + s3;

```

```
endmodule
```

```
TB
```

```
module array_multiplier_TB;
```

```
    reg [3:0] a, b;
```

```
    wire [7:0] product;
```

```
    array_multiplier uut (
```

```
        .a(a),
```

```
        .b(b),
```

```
        .product(product)
```

```
    );
```

```
    initial begin
```

```
        a = 4'd3; b = 4'd2; #10;
```

```
        a = 4'd4; b = 4'd5; #10;
```

```
        a = 4'd7; b = 4'd3; #10;
```

```
        a = 4'd8; b = 4'd8; #10;
```

```
        a = 4'd15; b = 4'd15; #10;
```

```
        $finish;
```

```
    end
```

```
endmodule
```

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns
> a[3:0]	f	3	4	7	8	f
> b[3:0]	f	2	5	3	8	f
> product[7:0]	e1	06	14	15	40	e1

35. Divider using Repeated Subtraction

```
module divider_subtract (
```

```
    input  [3:0] dividend,
```

```

input    [3:0] divisor,
output reg [3:0] quotient,
output reg [3:0] remainder
);

integer i;
reg [3:0] temp_dividend;

always @(*) begin
    quotient = 0;
    remainder = 0;
    temp_dividend = dividend;

    if (divisor == 0) begin
        quotient = 4'b0000;
        remainder = dividend;
    end else begin
        while (temp_dividend >= divisor) begin
            temp_dividend = temp_dividend - divisor;
            quotient = quotient + 1;
        end
        remainder = temp_dividend;
    end
end
endmodule

```

TB

```

module divider_subtract_TB;

    reg [3:0] dividend, divisor;

    wire [3:0] quotient, remainder;

```



```

divider_subtract uut (
    .dividend(dividend),
    .divisor(divisor),
    .quotient(quotient),
    .remainder(remainder)
);

```

```

initial begin

```

```

    dividend = 4'd10; divisor = 4'd3; #10;

```

```

    dividend = 4'd15; divisor = 4'd4; #10;

```

```

    dividend = 4'd9; divisor = 4'd2; #10;

```

```

    dividend = 4'd8; divisor = 4'd0; #10;

```

```

    dividend = 4'd7; divisor = 4'd7; #10;

```

```

    $finish;

```

```

end

```

```

endmodule

```

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns
> dividend[3:0]	7	a	f	9	8	7
> divisor[3:0]	7	3	4	2	0	7
> quotient[3:0]	1		3	4	0	1
> remainder[3:0]	0	1	3	1	8	0

30. B Flip Flop

```

module d_ff (

```

```

    input d,

```

```

    input clk,

```

```

    output reg q

```

```

);

```

```

    always @(posedge clk)

```

```

        q <= d;
    endmodule

TB
module d_ff_TB;

    reg d, clk;
    wire q;

    d_ff uut (
        .d(d),
        .clk(clk),
        .q(q)
    );

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin
        d = 0; #10;
        d = 1; #10;
        d = 0; #10;
        d = 1; #10;
        d = 1; #10;
        d = 0; #10;
        $finish;
    end

end
endmodule

```



```

    clk = 0;

    forever #5 clk = ~clk;

end

```

```

initial begin

```

```

    t = 0; #10;

```

```

    t = 1; #10;

```

```

    t = 1; #10;

```

```

    t = 0; #10;

```

```

    t = 1; #10;

```

```

    t = 1; #10;

```

```

    $finish;

```

```


end

```

```

endmodule

```

 

38. JK Flip Flop

```

module jk_ff(
    input j, k, clk,
    output reg q
);

always @(posedge clk) begin
    case ({j, k})
        2'b00: q <= q;
        2'b01: q <= 0;
        2'b10: q <= 1;

```

```
        2'b11: q <= ~q;
    endcase
end
```

```
endmodule
```

```
TB
```

```
module jk_ff_TB;
```

```
    reg j, k, clk;
```

```
    wire q;
```

```
    jk_ff uut (
```

```
        .j(j),
```

```
        .k(k),
```

```
        .clk(clk),
```

```
        .q(q)
```

```
    );
```

```
    initial begin
```

```
        clk = 0;
```

```
        forever #5 clk = ~clk;
```

```
    end
```

```
    initial begin
```

```
        j = 0; k = 0; #10;
```

```
        j = 0; k = 1; #10;
```

```
        j = 1; k = 0; #10;
```

```
        j = 1; k = 1; #10;
```

```
        j = 0; k = 1; #10;
```


```
        j = 1; k = 1; #10;
```

```
    $finish;
```

```

end
endmodule

```

 

39. SR Flip Flop

```

module sr_ff (
    input s, r, clk,
    output reg q
);
    always @(posedge clk) begin
        case ({s, r})
            2'b00: q <= q;
            2'b01: q <= 0;
            2'b10: q <= 1;
            2'b11: q <= 1'bx; // Invalid condition
        endcase
    end
endmodule

TB
module sr_ff_TB;
    reg s, r, clk;
    wire q;

    sr_ff uut (
        .s(s),
        .r(r),

```

```

        .clk(clk),
        .q(q)
    );


    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

```

```

    initial begin
        s = 0; r = 0; #10;
        s = 1; r = 0; #10;
        s = 0; r = 1; #10;
        s = 1; r = 1; #10;
        s = 0; r = 0; #10;
        $finish;
    end
endmodule

```

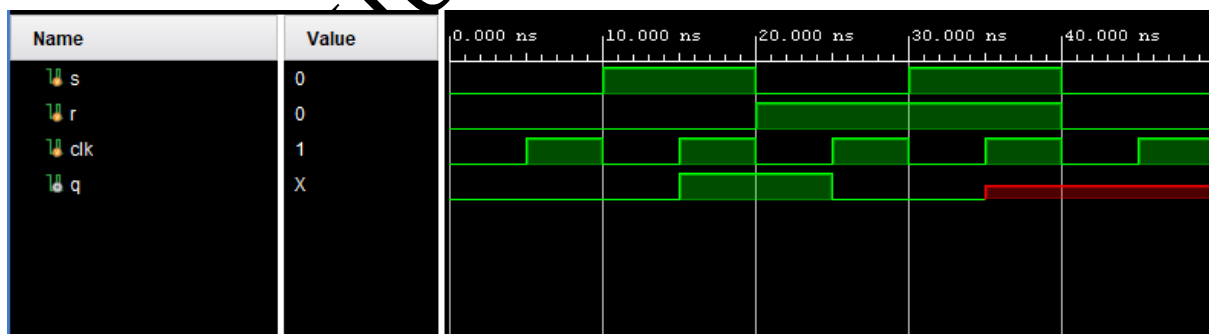

40. Master-Slave Flip-Flop

```

module ms_d_ff(
    input d, clk,
    output reg q
);

```

```
reg master;
```

```
always @(posedge clk)
```

```
    master <= d;
```

```
always @(negedge clk)
```

```
    q <= master;
```

```
endmodule
```

```
TB
```

```
module ms_d_ff_TB;
```

```
    reg d, clk;
```

```
    wire q;
```

```
    ms_d_ff uut (
```

```
        .d(d),
```

```
        .clk(clk),
```

```
        .q(q)
```

```
    );
```

```
    initial begin
```

```
        clk = 0;
```

```
        forever #5 clk = ~clk;
```

```
    end
```

```
    initial begin
```

```
        d = 0; #10;
```

```
        d = 1; #10;
```

```
        d = 0; #10;
```

```
        d = 1; #10;
```



```

    d = 1; #10;


    d = 0; #10;

    $finish;

end

endmodule

```

 

41. 4-bit Register with Positive Clock Edge

```

module reg4bit(
    input [3:0] d,
    input clk,
    output reg [3:0] q
);

```

```

    always @(posedge clk)
        q <= d;

```

```

endmodule

```

TB

```

module reg4bit_TB;

```

```
    reg [3:0] d;
```

```
    reg clk;
```

```
    wire [3:0] q;
```

```
    reg4bit uut (
```

```
        .d(d),
```

```

        .clk(clk),
        .q(q)
    );

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end


```

```

    initial begin
        d = 4'b0000; #10;
        d = 4'b1010; #10;
        d = 4'b1111; #10;
        d = 4'b0101; #10;
        d = 4'b0011; #10;
        $finish;
    end

endmodule

```

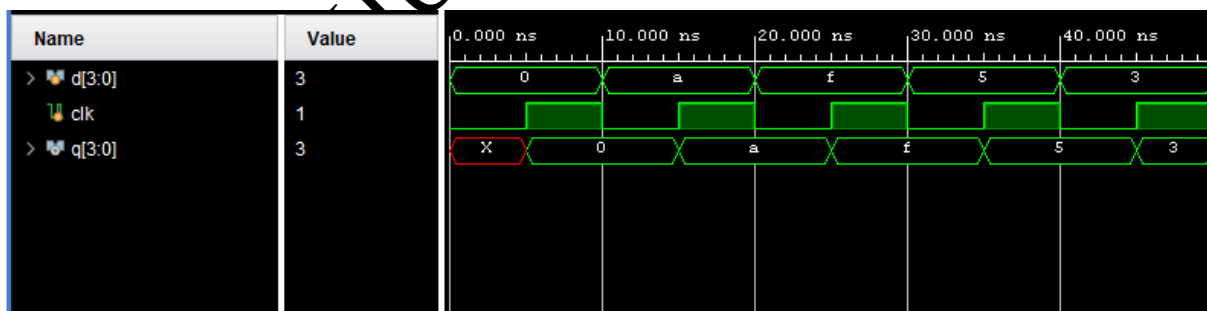

4.2. 4-bit Shift Register (Left)

```

module shift_register_left(
    input clk,
    input rst,
    input in,
    output reg [3:0] q

```

);

always @(posedge clk or posedge rst) begin

if (rst)

q <= 4'b0000;

else

q <= {q[2:0], in};

end

endmodule

TB

module shift_register_left_TB;

reg clk;

reg rst;

reg in;

wire [3:0] q;

shift_register_left uut (

.clk(clk),

.rst(rst),

.in(in),

.q(q)

);

initial begin

clk = 0;

forever #5 clk = ~clk;

end

```
initial begin
```

```
    rst = 1; in = 0; #10;
```

```
    rst = 0; in = 1; #10;
```

```
    in = 0; #10;
```

```
    in = 1; #10;
```


```
    in = 1; #10;
```

```
    in = 0; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

 

43. 4-bit Shift Register (Right)

```
module shift_register_right(
```

```
    input clk,
```

```
    input rst,
```

```
    input in,
```

```
    output reg [3:0] q
```

```
);
```

```
always @(posedge clk or posedge rst) begin
```

```
    if (rst)
```

```
        q <= 4'b0000;
```

```
    else
```

```
        q <= {in, q[3:1]};
```

end

endmodule

TB

module shift_register_right_TB;

reg clk;

reg rst;

reg in;

wire [3:0] q;

shift_register_right uut (

.clk(clk),

.rst(rst),

.in(in),

.q(q)

);

initial begin

clk = 0;

forever #5 clk = ~clk;

end

initial begin

rst = 1; in = 0; #10;

rst = 0; in = 1; #10;

in = 0; #10;

in = 1; #10;

in = 1; #10;

in = 0; #10;


```

    $finish;

end

endmodule

```

 

44. Bidirectional Shift Register

```

module shift_register_bidir(
    input clk,
    input rst,
    input dir,    // 0 = left, 1 = right
    input in,
    output reg [3:0] q
);

always @(posedge clk or posedge rst) begin
    if (rst)
        q <= 4'b0000;
    else if (dir) // Right shift
        q <= {in, q[3:1]};
    else // Left shift
        q <= {q[2:0], in};
end

endmodule

TB
module shift_register_bidir_TB;

```


```
reg clk;  
reg rst;  
reg dir;  
reg in;  
wire [3:0] q;
```

```
shift_register_bidir uut (  
    .clk(clk),  
    .rst(rst),  
    .dir(dir),  
    .in(in),  
    .q(q)  
);
```

```
initial begin  
    clk = 0;  
    forever #5 clk = ~clk;  
end
```

```
initial begin  
    rst = 1; dir = 0; in = 0; #10;  
    rst = 0;  
    in = 1; #10; // left shift in 1  
    in = 0; #10; // left shift in 0  
    dir = 1;  
    in = 1; #10; // right shift in 1  
    in = 0; #10; // right shift in 0  
    $finish;  
end
```

endmodule

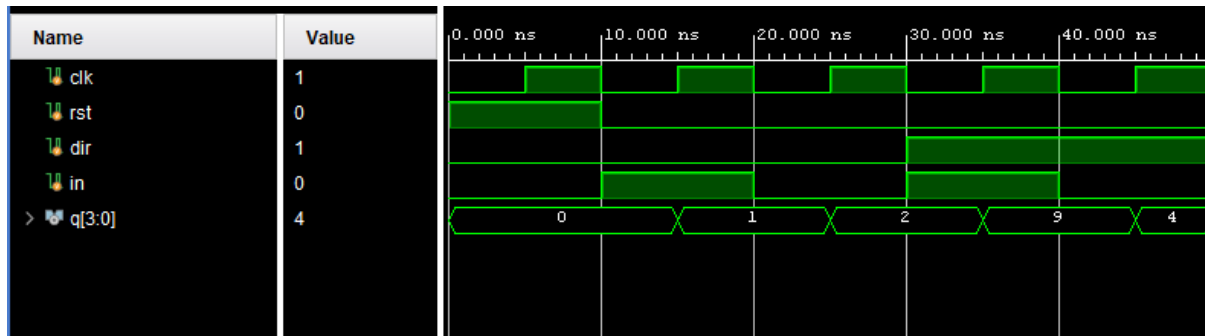

45. Parallel-In Parallel-Out Register

module pipo_register (

input clk,

input rst,

input [3:0] d,

output reg [3:0] q

);

always @(posedge clk or posedge rst) begin

if (rst)

q <= 4'b0000;

else

q <= d;

end

endmodule

TB

module pipo_register_TB;

reg clk;

reg rst;

reg [3:0] d;

wire [3:0] q;


```
pipo_register uut (
```

```
    .clk(clk),
```

```
    .rst(rst),
```

```
    .d(d),
```

```
    .q(q)
```

```
);
```

```
initial begin
```

```
    clk = 0;
```

```
    forever #5 clk = ~clk;
```

```
end
```

```
initial begin
```

```
    rst = 1; d = 4'b0000; #10;
```

```
    rst = 0; d = 4'b1010; #10;
```


```
    d = 4'b1100; #10;
```

```
    d = 4'b0111; #10;
```

```
    $finish;
```

```
end
```

```
endmodule
```

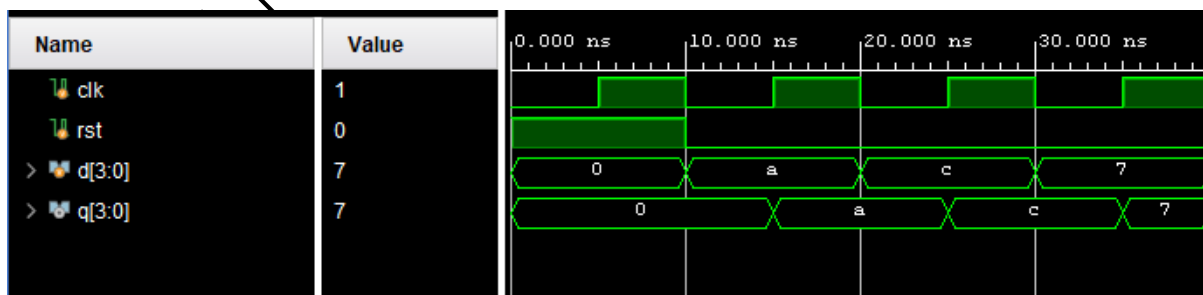

46. 4-bit Asynchronous Counter

```
module async_counter_4bit (
```

```
    input clk,
```

```
    input rst,
```

```
output reg [3:0] count  
);  
  
always @(negedge clk or posedge rst) begin  
    if (rst)  
        count <= 4'b0000;  
    else  
        count <= count + 1;  
end
```

```
endmodule
```

```
TB
```

```
module tb_async_counter_4bit;
```

```
reg clk, rst;
```

```
wire [3:0] count;
```

```
async_counter_4bit uut (
```

```
    .clk(clk),
```

```
    .rst(rst),
```

```
    .count(count)
```

```
);
```

```
initial begin
```

```
    clk = 0;
```

```
    forever #5 clk = ~clk;
```

```
end
```

```
initial begin
```

```

    rst = 1;

    #10 rst = 0;

    #100 $finish;


end

```

```

endmodule

```

 

47. 4-bit Synchronous Counter

```

module sync_counter_4bit(
    input clk,
    input rst,
    output reg [3:0] count
);

```

```

    always @(posedge clk or posedge rst) begin

```

```

        if (rst)

```

```

            count <= 4'b0000;

```

```

        else

```

```

            count <= count + 1;

```

```

        end

```

```

    endmodule

```

TB

```

module sync_counter_4bitTB;

```

```

    reg clk, rst;

```

```

    wire [3:0] count;

```

```

sync_counter_4bit uut (
    .clk(clk),
    .rst(rst),
    .count(count)
);

```

```

initial begin

```

```
    clk = 0;

```

```
    forever #5 clk = ~clk;

```

```
end

```

```

initial begin

```

```
    rst = 1;

```

```
    #10 rst = 0;

```

```
    #100 $finish;


```

```
end

```

```
endmodule

```

 

48. Up Counter

```

module up_counter(

```

```
    input clk,

```

```
    input rst,

```

```
    output reg [3:0] count

```

```
);

```

```
always @(posedge clk or posedge rst) begin
```

```
    if (rst)
```

```
        count <= 4'b0000;
```

```
    else
```

```
        count <= count + 1;
```

```
end
```

```
endmodule
```

```
TB
```

```
module up_counterTB;
```

```
    reg clk, rst;
```

```
    wire [3:0] count;
```

```
    up_counter uut (
```

```
        .clk(clk),
```

```
        .rst(rst),
```

```
        .count(count)
```

```
    );
```

```
    initial begin
```

```
        clk = 0;
```

```
        forever #5 clk = ~clk;
```

```
    end
```

```
    initial begin
```


```
        rst = 1;
```

```
        #10 rst = 0;
```

```
        #100 $finish;
```

end

endmodule

 

49. Down Counter

```
module down_counter(
```

```
    input clk,
```

```
    input rst,
```

```
    output reg [3:0] count
```

```
);
```

```
always @(posedge clk or posedge rst) begin
```

```
    if (rst)
```

```
        count <= 4'b1111;
```

```
    else
```

```
        count <= count - 1;
```

```
end
```

```
endmodule
```

```
TB
```

```
module down_counterTB;
```

```
    reg clk, rst;
```

```
    wire [3:0] count;
```

```
    down_counter uut (
```

```
        .clk(clk),
```

```

        .rst(rst),
        .count(count)
    );

```

```

initial begin

```

```

    clk = 0;

```

```

    forever #5 clk = ~clk;

```

```

end

```

```

initial begin

```

```

    rst = 1;

```

```

    #10 rst = 0;

```

```

    #100 $finish;

```

```


end

```

```

endmodule

```

 

50. Up/Down Counter

```

module up_down_counter(

```

```

    input clk,

```

```

    input rst,

```

```

    input up_down, // 1: up, 0: down

```

```

    output reg [3:0] count

```

```

);

```

```

always @(posedge clk or posedge rst) begin

```

```

    if (rst)

```

```

        count <= 4'b0000;

    else if (up_down)
        count <= count + 1;

    else
        count <= count - 1;

end

endmodule

TB

module up_down_counterTB;

    reg clk, rst, up_down;
    wire [3:0] count;

    up_down_counter uut (
        .clk(clk),
        .rst(rst),
        .up_down(up_down),
        .count(count)
    );

    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end


    initial begin
        rst = 1; up_down = 1;
        #10 rst = 0;
    end

```



```
#50 up_down = 0;  
#50 $finish;  
end
```

```
endmodule
```

 

PRIYANSHU AGGARWAL 22104