 


VLSI DESIGN AND AUTOMATION SUMMER INTERNSHIP


WEEK 3 SUBMISSION

RESOURCE : [WEEK 3](#) (ENC and NETLIST files are here)


FSM (Finite State Machine) – Sequence Detector 1011





236

 

Combination Circuit – Full Adder

 

  Sequential Circuit – Traffic Light Control



PRIYANSHU AGGARWAL 22102236